

## Basic Electronics

### Assessed Problems 3

Hand in before your week 4 deadline.


**APS3.1** The diagram shows an ideal AC voltage source connected to a series RC circuit which is to be used as a filter.

- (a) Find an expression for the magnitude of the *gain* of the filter circuit. [1 mark]
- (b) Is this a low-pass or high-pass filter? Justify your answer. [1 mark]
- (c) Show that the cut-off frequency for the filter is given by [1 mark]

$$\omega_c = \frac{1}{RC}$$

For the rest of the question, assume  $R = 120\,\Omega$ ,  $C = 15.625\,\mu\text{F}$  and the AC voltage source has an amplitude 10V, frequency  $200/\pi$  Hz, and is a maximum at time  $t = 0$ .

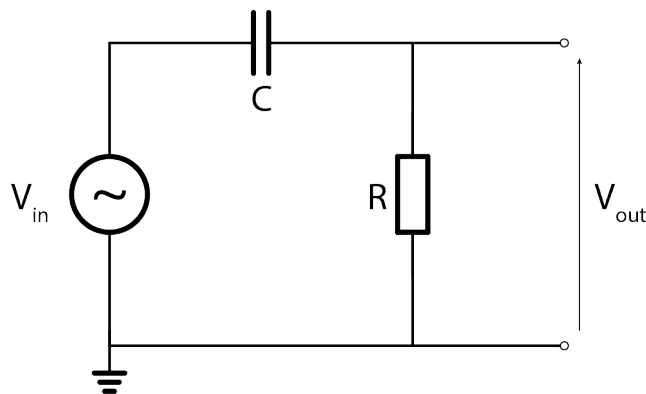- (d) Express the circuit's impedance in both complex cartesian and polar form. [1 mark]
- (e) Find the amplitudes of
  - i. the circuit current.
  - ii. the voltage across the resistor.
  - iii. the voltage across the capacitor. [3 marks]
- (f) Draw the capacitor and resistor voltages on a phasor diagram. Add a phasor representing the applied voltage. [1 mark]
- (g) Hence show that Kirchhoff's voltage law holds. [1 mark]
- (h) Does the output signal lead or lag the input? Explain your answer. [1 mark]



*Hint: It can be useful to represent the three voltages (input, capacitor and resistor) as functions of time and then plot these using Python. You can then check your answers against a simulation of the circuit in LTSpice. This is **not** required to be given as part of your answer, however.*

CC  
8-Jan-18


## Basic Electronics

### *Tutorial Problems 3*

These problems are for your week 4 tutorial

---

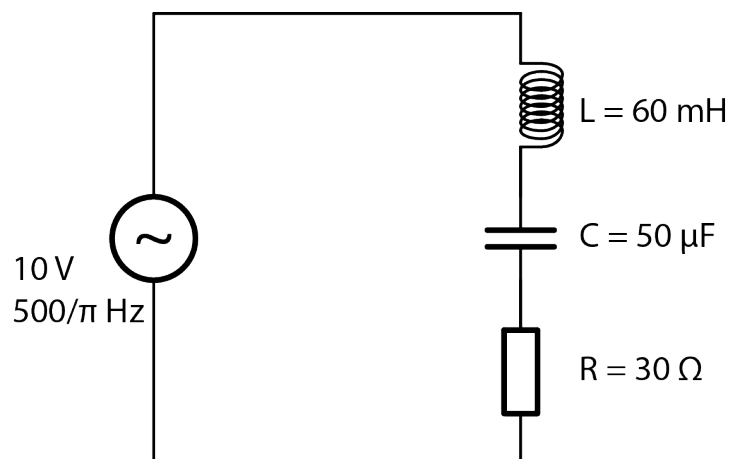
1. A series LCR circuit comprising a  $30\,\Omega$  resistor,  $50\,\mu\text{F}$  capacitor and  $60\,\text{mH}$  inductor is connected to an ideal  $10\,\text{V}$  sinusoidal source operating at a frequency of  $500/\pi\,\text{Hz}$ .
  - (a) Write an expression for the complex impedance of the LCR circuit.
  - (b) Find the amplitude of the potential difference across
    - i. the resistor,
    - ii. the capacitor,
    - iii. the inductor.
  - (c) Sketch these three as phasors in the complex plane.
  - (d) What is the average power delivered by the source?
  - (e) Find the peak energy stored by
    - i. the capacitor,
    - ii. the inductor.



---

**Discussion Problems**

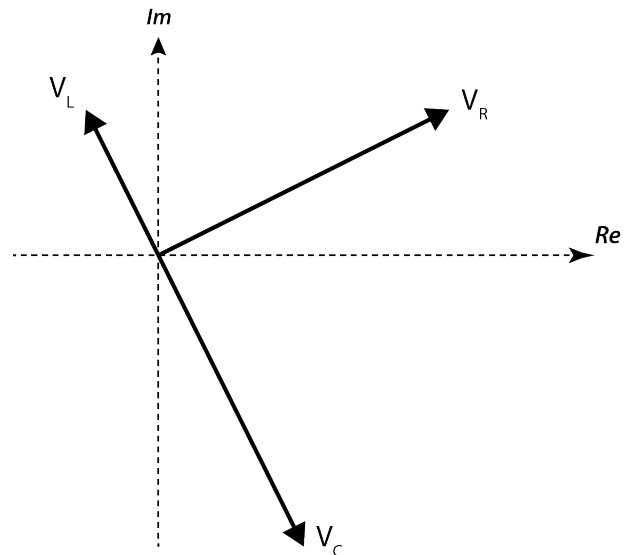2. The figure below shows the phasor diagram for a series LCR circuit. We **don't** know the component values or the driving frequency.
- (a) Is the driving frequency above, below or at the resonant frequency?
  - (b) Add a phasor representing the amplitude of the applied voltage.




3. Consider a circuit similar to question 1 but where the resistor, capacitor and inductor are in **parallel**. At  $\omega = \omega_0 = 1/\sqrt{LC}$ , will the magnitude of the impedance be a maximum or a minimum? Contrast this with the series LCR circuit.
-


## Basic Electronics

### Further Problems 3

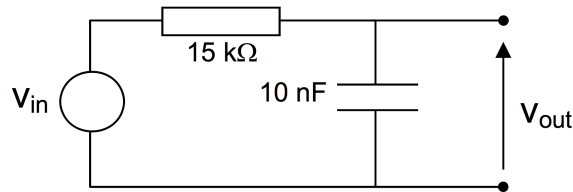1. The ideal source  $V_{in}$  applies a sine wave voltage of amplitude 3 V and angular frequency 12566 rad/s to the RC filter shown below. What is the magnitude of the output voltage and what is its phase angle relative to the input?



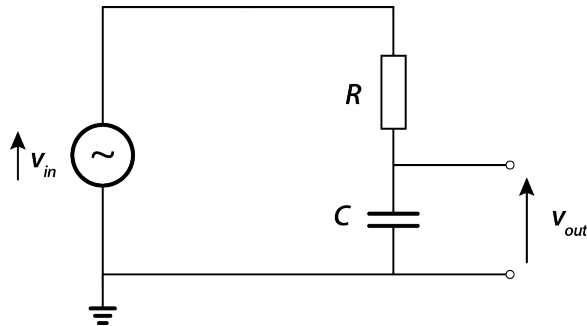
2. A low-pass filter is formed from a 100 kΩ resistor in series with a 100 pF capacitor. The RMS voltage across the capacitor is found to be 2 V and lags the input voltage  $V_{in}$  by  $\pi/4$  rad. Which of the following statements about  $V_{in}$  is true?
- $V_{in} = 2\sqrt{2} V_{RMS}$  and  $f = 10^5$  Hz
  - $V_{in} = 2\sqrt{2} V_{RMS}$  and  $f = 6.28$  MHz
  - $V_{in}$  has an amplitude of 4 V and  $\omega = 10^5$  rad/s
  - $V_{in}$  has a peak-to-peak amplitude of  $4\sqrt{2}$  V and  $\omega = 10^5$  rad/s
  - $V_{in}$  has a peak-to-peak amplitude of 8 V and  $\omega = 100$  rad/s
3. The figure below shows a RC filter circuit. The sinusoidal input waveform has an amplitude of 2 volts and a phase angle zero at time  $t = 0$ . Assume the same angular frequency  $\omega = 1/RC$  for all parts of this question.



- Show that the output amplitude is  $\sqrt{2}$  volts.
- Calculate the phase difference, in radians, between the output waveform and the input. Does the output lead or lag the input?
- Sketch the input and output phasors on a phasor diagram.
- The capacitor is replaced by an inductor. Find an expression for the inductance  $L$  which will result in the same output amplitude.

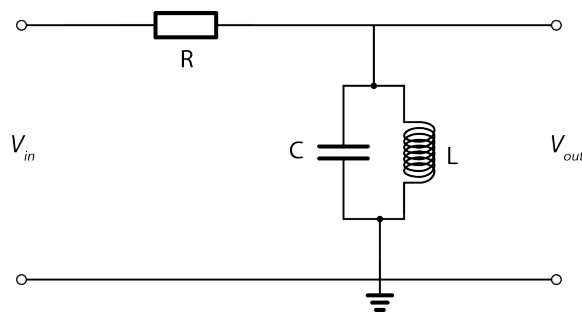4. The figure below shows a LCR filter circuit.

- Find an expression for the magnitude of the filter's gain.
- What is the gain for very low and very high frequencies? For the natural frequency  $\omega = \omega_0$ ?
- Explain this behaviour, in terms of the individual component impedances at these frequencies.
- Hence describe what type of filter this is.
- Find an expression for the bandwidth of the filter.
- For  $C = 1000 \mu\text{F}$ ,  $L = 1 \text{ mH}$  and  $R = 10 \Omega$ , find the natural frequency and the bandwidth.
- Describe how to double the bandwidth without changing the natural frequency.




---

*Numerical solutions and hints*

- Amplitude 1.41 V Phase -1.08 rad.
- (c)
- (b)  $-\frac{\pi}{4}$  rad, (d)  $L = R^2 C$
- (b) Zero and 1, (f) 1000 and 100 rad/s.